

Multiplexer




MUX

Multiplexer


- **Multiplexer (Selector)**

- 2^n data inputs
- n control inputs
- 1 output
- Described as $2^n:1$
- Is used to connect only one of 2^n inputs to a single output at a given time
- The control signal pattern forms the binary index of the input connected to the output
- Called "MUX" for brevity


A	Z
0	0
1	1

   

Multiplexer

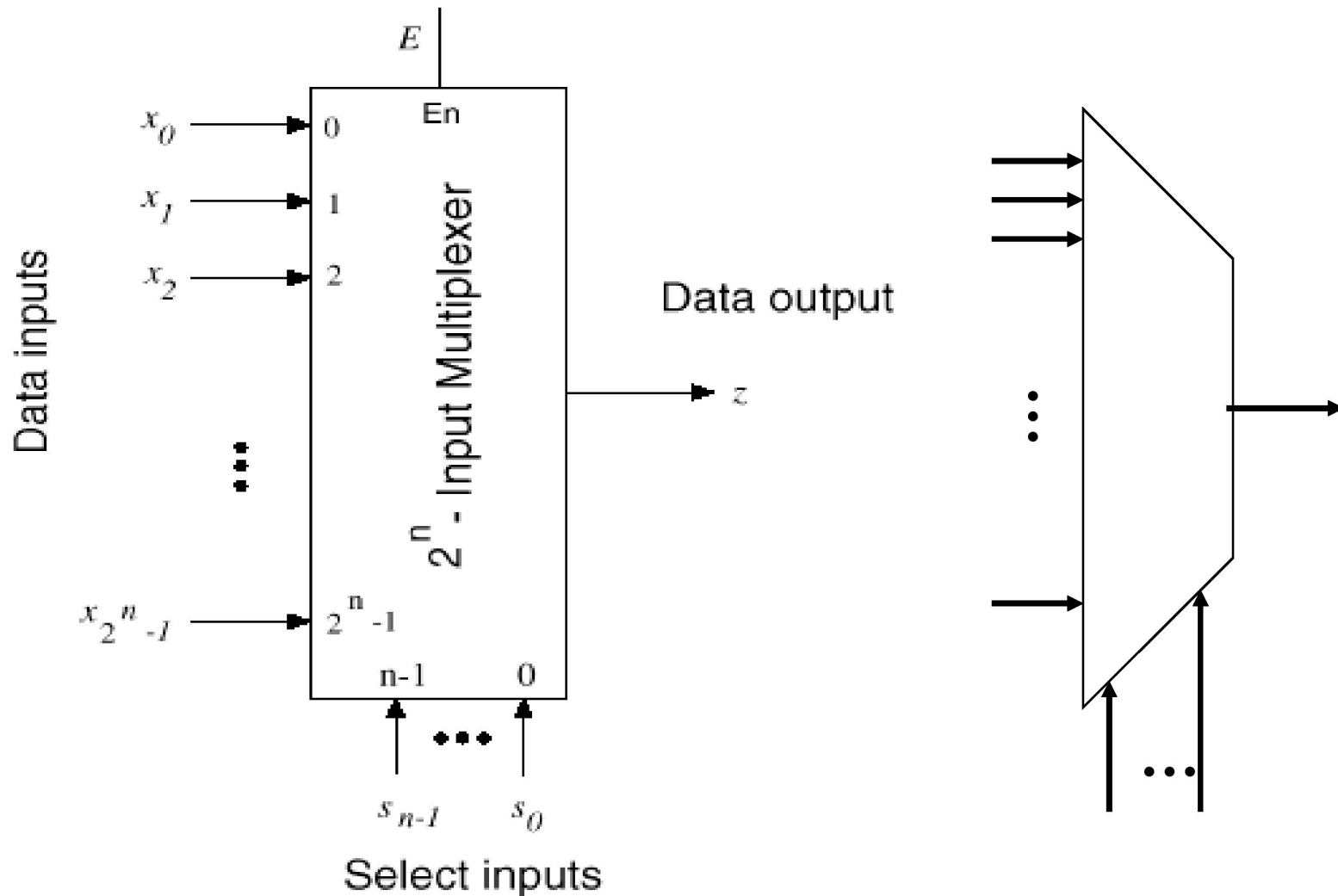


MUX Boolean Functions

 

$$Z = A' I_0 + A I_1$$


		A			
I ₁	00	01	11	10	
0	0	1	0	0	
1	0	1	1	1	

Diagram illustrating the truth table for the 2:1 MUX output Z. The inputs are A (select) and I₁ (data). The output Z is 1 for the combinations (A, I₁) = (0, 1), (1, 1), and (1, 0). The output Z is 0 for (A, I₁) = (0, 0) and (1, 1). The output Z is 1 for (A, I₁) = (0, 1) and (1, 1). The output Z is 0 for (A, I₁) = (0, 0) and (1, 0).

 

		A	
B	0	1	
0	I ₀	I ₂	
1	I ₁	I ₃	
 
$$Z = A' B' I_0 + A' B I_1 + A B' I_2 + A B I_3$$




$$Z = A' B' C' I_0 + A' B' C I_1 + A' B C' I_2 + A' B C I_3 + A B' C' I_4 + A B' C I_5 + A B C' I_6 + A B C I_7$$

In general: $Z = \sum_{k=0}^{2^n-1} m_k I_k$, in minterm form

Circuit Diagram

 - 4:1 MUX


$$Y = A' B' I_0 + A' B I_1 + A B' I_2 + A B I_3$$




A	B	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

Cascading MUXes

 - Design an 8:1 MUX by using smaller MUXes



Another Implementation

 


Larger Data Lines

- What if we want to select m -bit datawords?
- Combine MUX blocks in parallel with common select and enable signals


4-bit data

 - **Example:**

- Selection between 2 sets of 4-bit inputs ($x[3:0]$ or $y[3:0]$)
- Use four 2:1 MUXes in parallel
- Tie all four control lines together
- Connect $x[3:0]$ to I_0 s and $y[3:0]$ to I_1 s



Application

 


Adder with multiple input sources:

$A+C$ or
 $A+D$ or
 $B+C$ or
 $B+D$

MUX by 3-State Buffers

Three-state logic in place of AND-OR

 

(b)
Output of gates can be connected

General Logic by MUX


- Any Boolean function of n variables can be implemented using a $2^{n-1}:1$ multiplexer
- $n-1$ inputs go to the control lines directly
- One input is used to appropriately determine the output
- The choice of the singled-out input doesn't change the functionality but it affects the complexity
- MUXes can only implement **single-output functions**

General Logic by MUX

 • Example:


$$F = A' B' C' + A' B C' + A B C' + A B C$$

$$= A' B' (C') + A' B (C') + A B' (0) + A B (1)$$



A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

A	B	F
0	0	C'
0	1	C'
1	0	0
1	1	1

 

What if A or B had been chosen as the singled-out input?

Using Smaller MUX

- How about implementing a 4-variable function by a 4:1 MUX
 - Can still be done
 - 2 input variables go to the 2 control lines directly
 - The other 2 input variables will go to the MUX inputs using some necessary gates
 - Choose the 2 that go to control inputs and the 2 that go to the MUX inputs carefully!
 - The choice affects the number of necessary gates

General Logic

- **By decoder:**

- **Multiple outputs:**

- A single decoder
 - One OR gate for each output

- **By MUX:**

- **Multiple outputs:**

- One MUX needed for each output
 - No need for OR gates

- **Use MUX for single-output functions**


- **Use decoder for multiple-output functions**

Standard MSI MUXes

- 74x151

8:1 MUX

Inputs				Outputs	
EN_L	C	B	A	Y	Y_L
1	x	x	x	0	1
0	0	0	0	D0	D0'
0	0	0	1	D1	D1'
0	0	1	0	D2	D2'
0	0	1	1	D3	D3'
0	1	0	0	D4	D4'
0	1	0	1	D5	D5'
0	1	1	0	D6	D6'
0	1	1	1	D7	D7'

 


Standard MSI MUXes

- **74x157**

◀ 4-bit wide, 2:1 MUX


<i>Inputs</i>		<i>Outputs</i>			
G_L	S	1Y	2Y	3Y	4Y
1	x	0	0	0	0
0	0	1A	2A	3A	4A
0	1	1B	2B	3B	4B

 


Demultiplexer

DEMUX

DEMUX

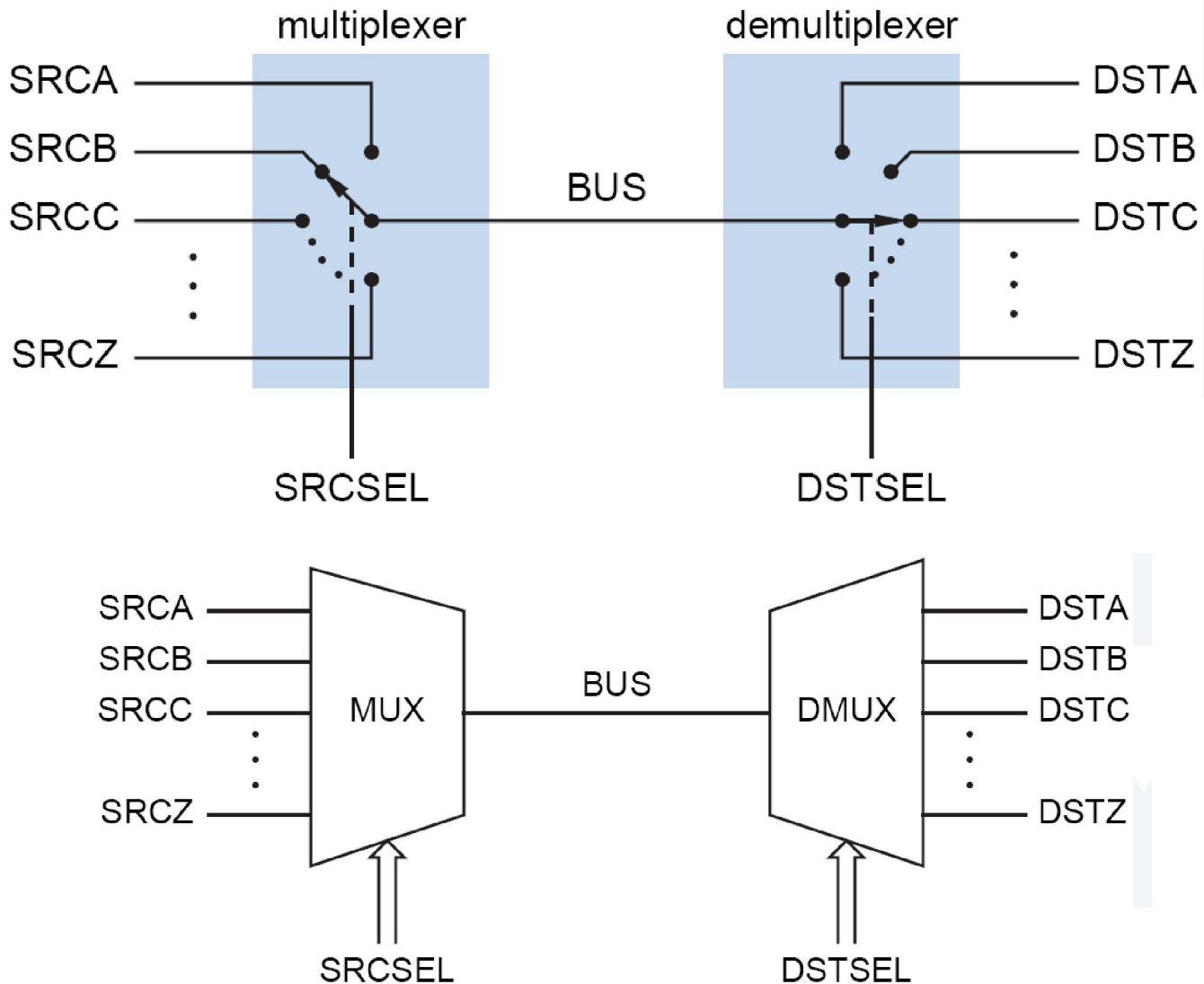

Decoder vs. DEMUX

 

E	A	B	C	O_0	O_1	O_2	O_3	O_4	O_5	O_6	O_7
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	1

By switching the view between (A, B, C) and E, can a decoder be considered a DEMUX?

Decoder vs. DEMUX

