

Hardware Description Language

HDL


Hardware Description Language

- **HDL**
 - Describes circuits and systems in text.
 - As a software program.
 - Can be processed by computers.
 - VHDL, Verilog, AHDL, SystemC.
- **Applications:**
 - Simulation
 - Synthesis

Simulation and Synthesis

- **Simulation**

 - Input waveform and circuit description --> Output waveform
- Predicts circuit behavior before fabrication (debug before physical implementation).



Verilog HDL

- Verilog or VHDL?
 - Similar concepts, different syntax
- Similar to C/C++ Syntax
 - Case sensitive,
 - Comments: //
 - ; at the end of each statement

Example

- **module:**
 - Hardware component
- **Ports:**
 - As function parameters
 - But must specify input or output
- **wire:**
 - Intermediate signals

```
//HDL Example 3-1
//-----
module smpl_circuit(A,B,C,x,y);
  input A,B,C;
  output x,y;
  wire e;
  and g1(e,A,B);
  not g2(y,C);
  or g3(x,e,y);
endmodule
```


 


Fig. 3-37 Circuit to Demonstrate HDL

- **Concurrent Execution**
 - Order not important.

Example

 

```
//HDL Example 3-1
//-----
module smpl_circuit(A,B,C,x,y);
  input A,B,C;
  output x,y;
  wire e;
  and g1(e,A,B);
  not g2(y, C);
  or g3(x,e,y);
endmodule
```

- **Concurrent Execution**
 - Order not important.

Delays

- **Timescale:**
 - ``timescale 1ns/100ps`
 - `1ns`: time unit
 - `100ps`: precision (unit used for rounding)
 - Default: 1ns/100ps (0.1 ns)
- **Gate Delays:**
 - Used by simulator to generate correct waveforms

Delays

```
//HDL Example 3-2
//-----
//Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
  input A,B,C;
  output x,y;
  wire e;
  and #(30) g1(e,A,B);
  or #(20) g3(x,e,y);
  not #(10) g2(y,C);
endmodule
```

 


Fig. 3-37 Circuit to Demonstrate HDL

Testbench

- **Testbench:**
 - Program written to test the circuit
 - Sets the input values,
 - Changes them over time.
 - Instantiates the module(s).
 - Inputs by **reg** (generally in sequential constructs)
 - Outputs by **wire**

Testbench Example

```
//HDL Example 3-3
//-----
//Stimulus for simple circuit
module stimcrct;
  reg A,B,C;
  wire x,y;
  circuit_with_delay cwd(A,B,C,x,y);
  initial
    begin
      A = 1'b0; B = 1'b0; C = 1'b0;
      #100
      A = 1'b1; B = 1'b1; C = 1'b1;
      #100 $finish;
    end
endmodule

//Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
  input A,B,C;
  output x,y;
  wire e;
  and # (30) g1(e,A,B);
  or # (20) g3(x,e,y);
  not # (10) g2(y,C);
endmodule
```

Testbench:

- Doesn't have port.
- Instantiation.
- `<size>'<base><value>`
 - Base: b, o, d, h.
- ABC = “000” → “111”
- 100ns delay.
- Finishes at 200ns.

 


Fig. 3-37 Circuit to Demonstrate HDL

Testbench Example

 


Fig. 3-37 Circuit to Demonstrate HDL

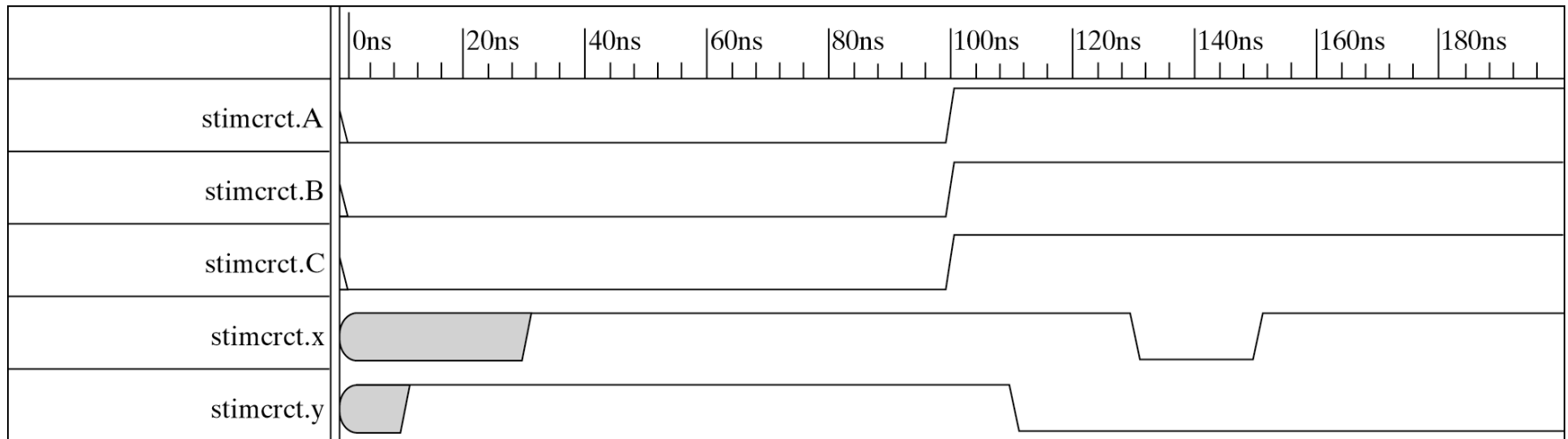


Fig. 3-38 Simulation Output of HDL Example 3-3

Primitives

- **Built-in Primitives:**
 - and, or, not, nand, nor, xor, xnor, buf.
- **User-Defined Primitives (UDP):**
 - User can define by truth table.

Simulation

- **ModelSim:**
 - An industrial and widely used simulator
 - \$25K