

Verilog

Behavioral Description

- **initial:**
 - is executed once at the beginning.
- **always:**
 - is repeated until the end of simulation.

Clock Generation

➤ Two methods:

- 15 cycles of clock.
- clock period = 20 time units.

```
initial
begin
    clock = 1'b0;
    repeat (30)
        #10 clock = ~clock;
end
```

```
initial
begin
    clock = 1'b0;
    #300 $finish;
end

always
    #10 clock = ~clock;
```

? Description

- Output Q must be declared as **reg**.
- Inside **initial** and **always**, **if-else** and **case** statements can be used.

```
//HDL Example 5-1
//-----
//Description of xxxx (See Fig.5-6)
module xxxx (Q,D,control);
    output Q;
    input D,control;
    reg Q;
    always @ (control or D)
        if (control == 1) Q = D; //Same as: if (control)
endmodule
```

D-Latch Description

- Output Q must be declared as **reg**.
- Inside **initial** and **always**, **if-else** and **case** statements can be used.

```
//HDL Example 5-1
//-----
//Description of D latch (See Fig.5-6)
module D_latch (Q,D,control);
    output Q;
    input D,control;
    reg Q;
    always @ (control or D)
        if (control == 1) Q = D; //Same as: if (control)
endmodule
```

D Flip-Flop Description

```
//HDL Example 5-2
//-----
//D flip-flop
module D_FF (Q,D,CLK);
    output Q;
    input D,CLK;
    reg Q;
    always @ (posedge CLK)
        Q = D;
endmodule
```


D Flip-Flop Description

```
//HDL Example 5-2
//-----
//D flip-flop
module D_FF (Q,D,CLK) ;
    output Q;
    input D,CLK;
    reg Q;
    always @ (posedge CLK)
        Q = D;
endmodule
```

```
//D flip-flop with   reset.
module DFF (Q,D,CLK,RST) ;
    output Q;
    input D,CLK,RST;
    reg Q;
    always @ (posedge CLK or negedge RST)
        if (RST == 0) Q = 1'b0;    // Same as: if (~RST)
        else Q = D;
endmodule
```

T-FF Description (Structural)
 
```
//HDL Example 5-3
//-----
//T flip-flop from D flip-flop and gates
module TFF (Q,T,CLK,RST);
    output Q;
    input T,CLK,RST;
    wire DT;
    assign DT = Q ^ T ;
    //Instantiate the D flip-flop
    DFF TF1 (Q,DT,CLK,RST);
endmodule
```



(b) Conversion of D to T

JK-FF Description (Structural)

```
//JK flip-flop from D flip-flop and gates
module JKFF (Q,J,K,CLK,RST);
    output Q;
    input J,K,CLK,RST;
    wire JK;
    assign JK = (J & ~Q) | (~K & Q);
    //Instantiate D flipflop
    DFF JK1 (Q,JK,CLK,RST);
endmodule
```

JK-FF Description (Behavioral)

- **case** executes one of the statements.

```
//HDL Example 5-4
//-----
// Functional description of JK flip-flop
module JK_FF (J,K,CLK,Q,Qnot);
    output Q,Qnot;
    input  J,K,CLK;
    reg  Q;
    assign Qnot = ~ Q ;
    always @ (posedge CLK)
        case ({J,K})
            2'b00: Q = Q;
            2'b01: Q = 1'b0;
            2'b10: Q = 1'b1;
            2'b11: Q = ~ Q;
        endcase
endmodule
```

A Sequential Circuit: Schematic Diagram

 


Fig. 5-15 Example of Sequential Circuit

State Diagram (Behavioral)

 


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

Mealy (Behavioral)

```
module Mealy_md1 (x,y,CLK,RST);
```

```
  input x,CLK,RST;
```

```
  output y;
```

```
  reg y;
```

```
  reg [1:0] Prstate, Nxtstate;
```

```
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
```

```
  always @ (posedge CLK or negedge RST)
```

```
    if (~RST) Prstate = S0; //Initializ
```

```
    else Prstate = Nxtstate; //Clock ope
```

```
  always @ (Prstate or x) //Determine
```

```
    case (Prstate)
```

```
      S0: if (x) Nxtstate = S1;
```

```
          else Nxtstate = S0;
```

```
      S1: if (x) Nxtstate = S3;
```

```
          else Nxtstate = S0;
```

```
      S2: if (~x) Nxtstate = S0;
```

```
          else Nxtstate = S2;
```

```
      S3: if (x) Nxtstate = S2;
```

```
          else Nxtstate = S0;
```

```
    endcase
```

```
  always @ (Prstate or x) //Evaluate output
```

```
    case (Prstate)
```

```
      S0: y = 0;
```

```
      S1: if (x) y = 1'b0; else y = 1'b1;
```

```
      S2: if (x) y = 1'b0; else y = 1'b1;
```

```
      S3: if (x) y = 1'b0; else y = 1'b1;
```

```
    endcase
```

➤ parameter defines constants.


 



Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

Moore (Behavioral) (One always)


```
module Moore_md1 (x,AB,CLK,RST);  
  input x,CLK,RST;  
  output [1:0]AB;  
  reg [1:0] state;  
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;  
  always @ (posedge CLK or negedge RST)  
    if (~RST) state = S0; //Initialize to state S0  
    else  
  case (state)  
    S0: if (~x) state = S1; else state = S0;  
    S1: if (x) state = S2; else state = S3;  
    S2: if (~x) state = S3; else state = S2;  
    S3: if (~x) state = S0; else state = S3;  
  endcase  
  assign AB = state; //Output of flip-flops  
endmodule
```

 

Moore (Structural)

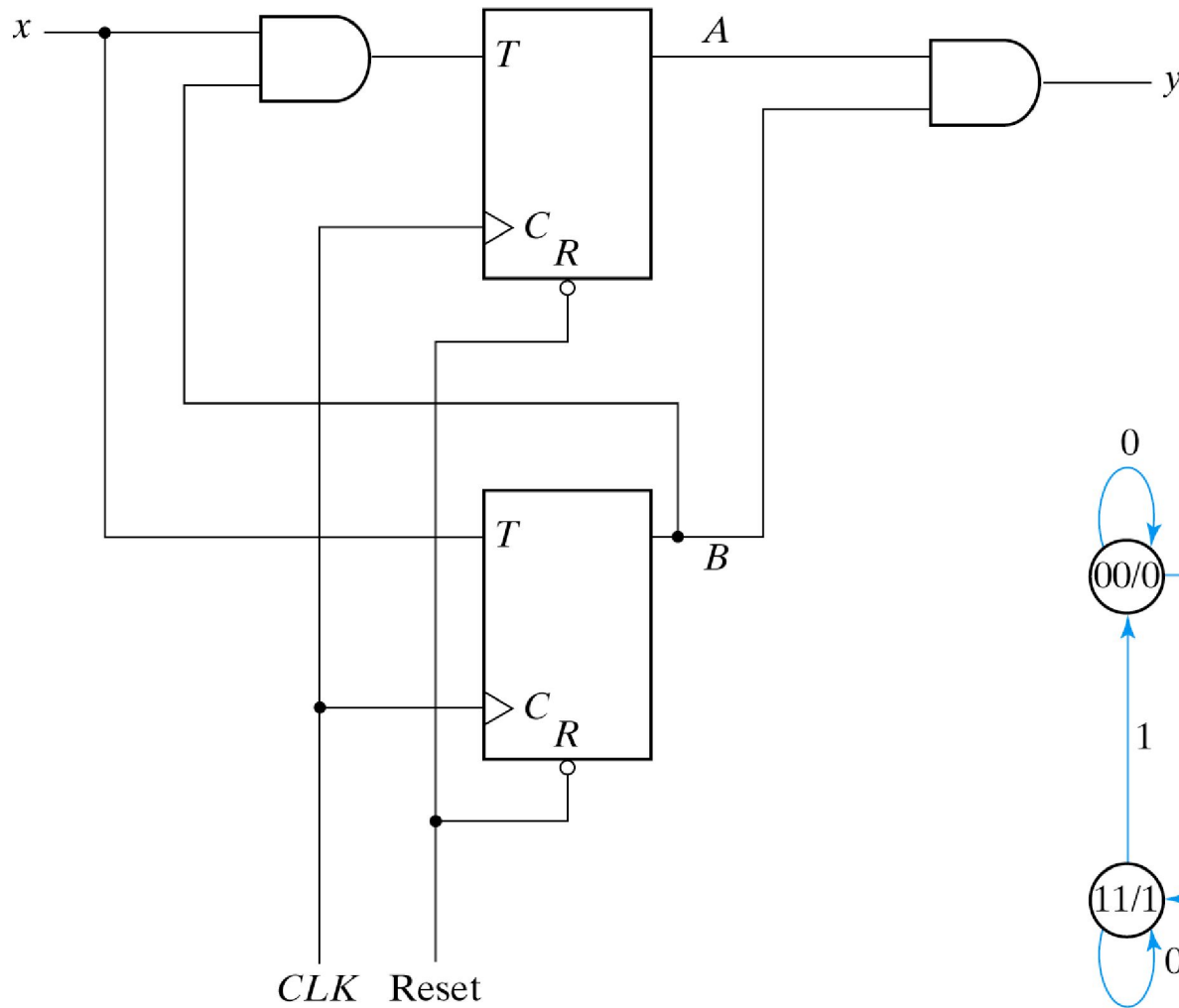

(a) Circuit diagram

 

(b) State diagram

Moore (Structural)

```


module Tcircuit (x,y,A,B,CLK,RST);
    input x,CLK,RST;
    output y,A,B;
    wire TA,TB;
    //Flip-flop input equations
    assign TB = x,
           TA = x & B;
    //Output equation
    assign y = A & B;
    //Instantiate T flip-flops
    T_FF BF (B,TB,CLK,RST);
    T_FF AF (A,TA,CLK,RST);
endmodule

```


```

//T flip-flop
module T_FF (Q,T,CLK,RST);
    output Q;
    input T,CLK,RST;
    reg Q;
    always @ (posedge CLK or negedge RST)
        if (~RST) Q = 1'b0;
        else Q = Q ^ T;
endmodule

```

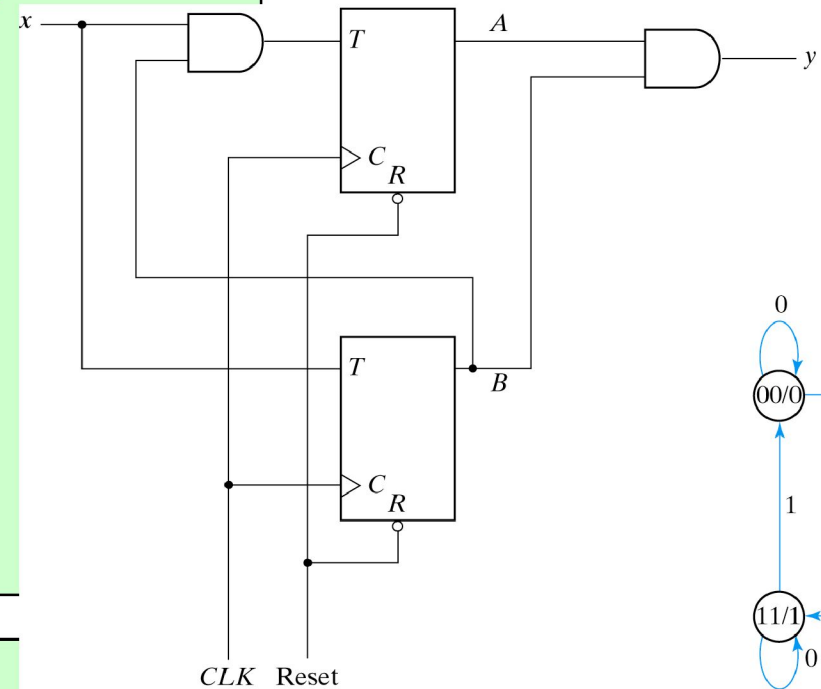

(a) Circuit diagram

 

(b) State diagram

Fig. 5-20 Sequential Circuit with *T* Flip-Flops

Testbench

```
//Stimulus for testing sequential circuit
module testTcircuit;
    reg x,CLK,RST; //inputs for circuit
    wire y,A,B;    //output from circuit
    Tcircuit TC (x,y,A,B,CLK,RST); // instantiate circuit
    initial
        begin
            RST = 0;
            CLK = 0;
            #5 RST = 1;
            repeat (16)
                #5 CLK = ~CLK;
            end
        initial
            begin
                x = 0;
                #15 x = 1;
                repeat (8)
                    #10 x = ~ x;
                end
            endmodule
```

Waveforms

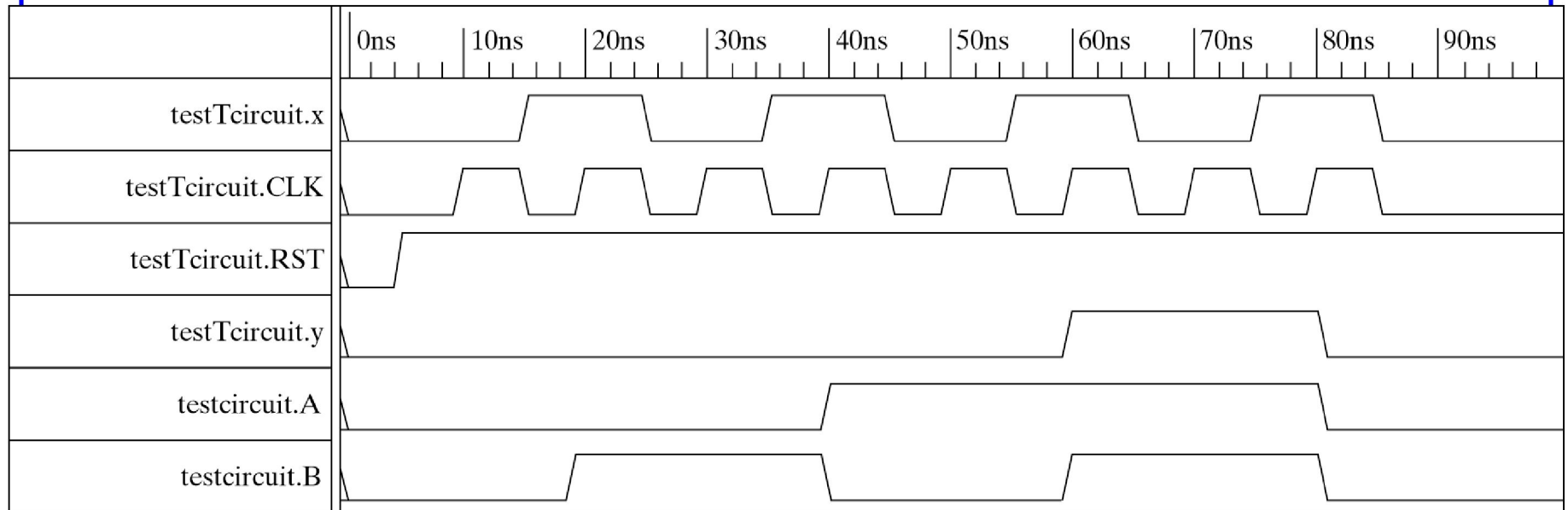


Fig. 5-21 Simulation Output of HDL Example 5-7