

# Read-Only Memory


## ROM

# ROM

- **Can be used:**
  - to implement any arbitrary combinational circuit
  - as a memory
- **Consists of:**
  - an  $n$ -to- $2^n$  decoder that produces ALL minterms
  - a set of programmable OR gates that produce SoP's
- **Is usually described in terms of:**
  - size of its decoder output (number of memory rows)
  - number of OR gates (memory width)
  - i.e.,  $2^n \times w$ , e.g.,  $8 \times 4$ ,  $1024 \times 8$ , etc.

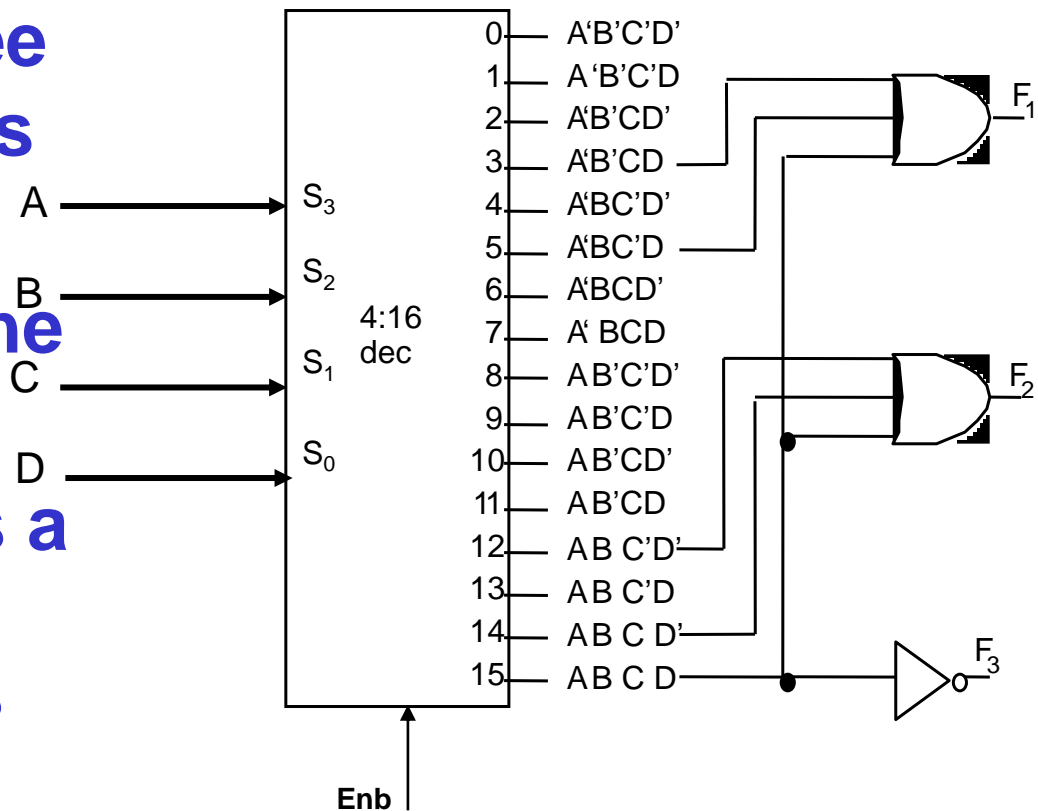
# ROM: Example 1

- A 4-to-16 decoder
- Three OR gates
- Implemented three Boolean functions
- Has an “enable” input to control the output
- Can be viewed as a 16 x 3 memory
- Memory content?



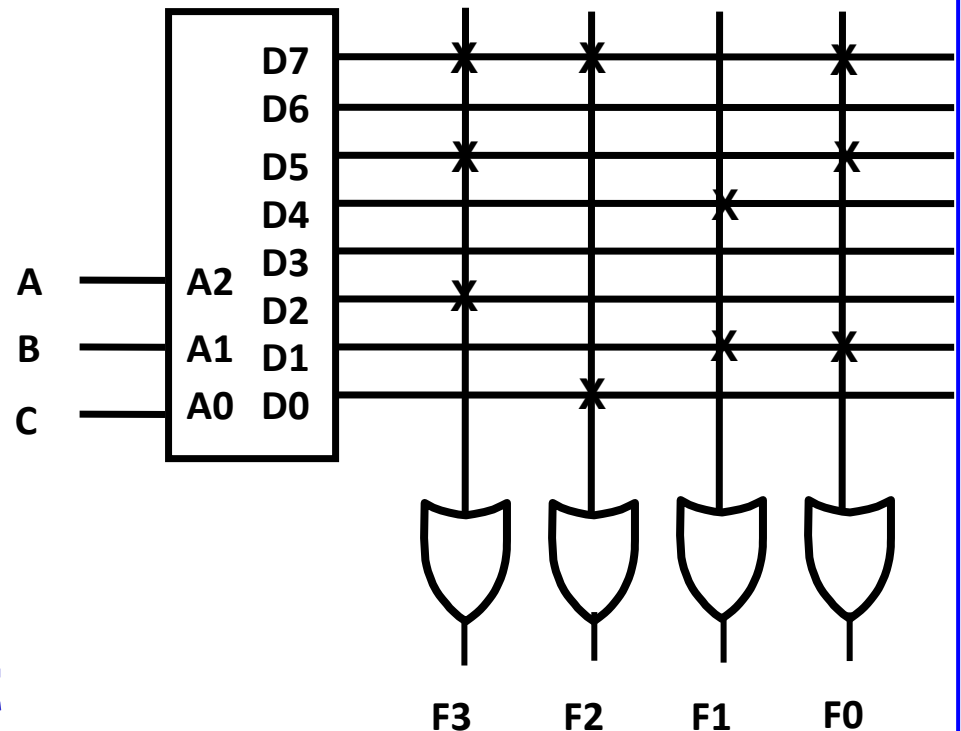
## ROM: Example 2


- A 3-to-8 decoder
- Four OR gates
- Can implement four Boolean functions
- Can be viewed as a 8 x 4 memory
- No “enable” input
- Memory content?




# ROM vs. PLA/PAL

 

(a) Programmable read-only memory (PROM)

 

 (b) Programmable array logic (PAL) device



(c) Programmable logic array (PLA) device

# General Logic Implementation

- Given a  $2^k \times n$  ROM, we can implement ANY combinational circuit with at most  $k$  inputs and at most  $n$  outputs.

- **Why?**

- $k$ -to- $2^k$  decoder will generate all  $2^k$  possible minterms
- Each of the OR gates can implement a  $\Sigma m()$
- Each  $\Sigma m()$  can be programmed to represent one function

# Example

- **Find a ROM-based circuit implementation for:**

- $f(a,b,c) = a'b' + abc$

- $g(a,b,c) = a'b'c' + ab + bc$


- $h(a,b,c) = a'b' + c$

- **Solution:**

1. Determine the required ROM size
2. Express  $f()$ ,  $g()$ , and  $h()$  in  $\Sigma m()$  format (use truth tables)
3. Program the ROM, based on the 3  $\Sigma m()$ 's

## Example (Continued)

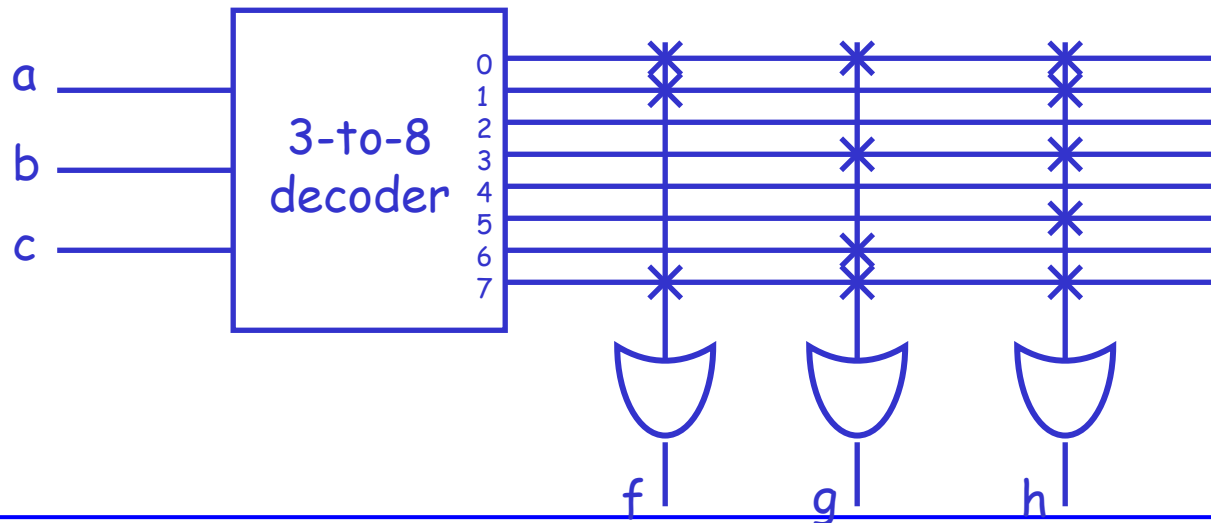1. There are 3 inputs and 3 outputs, thus we need an 8x3 ROM block.
2. Prepare the minterm lists:
  - $f = \sum m(0, 1, 7)$
  - $g = \sum m(0, 3, 6, 7)$
  - $h = \sum m(0, 1, 3, 5, 7)$
3. Program the ROM






# ROM as a Memory

- ROM's can be viewed as memory with the inputs as address lines, and outputs as the stored data
- Usually have:
  - N input lines,
  - M output lines,
  - Provide  $2^N \times M$  bits of memory
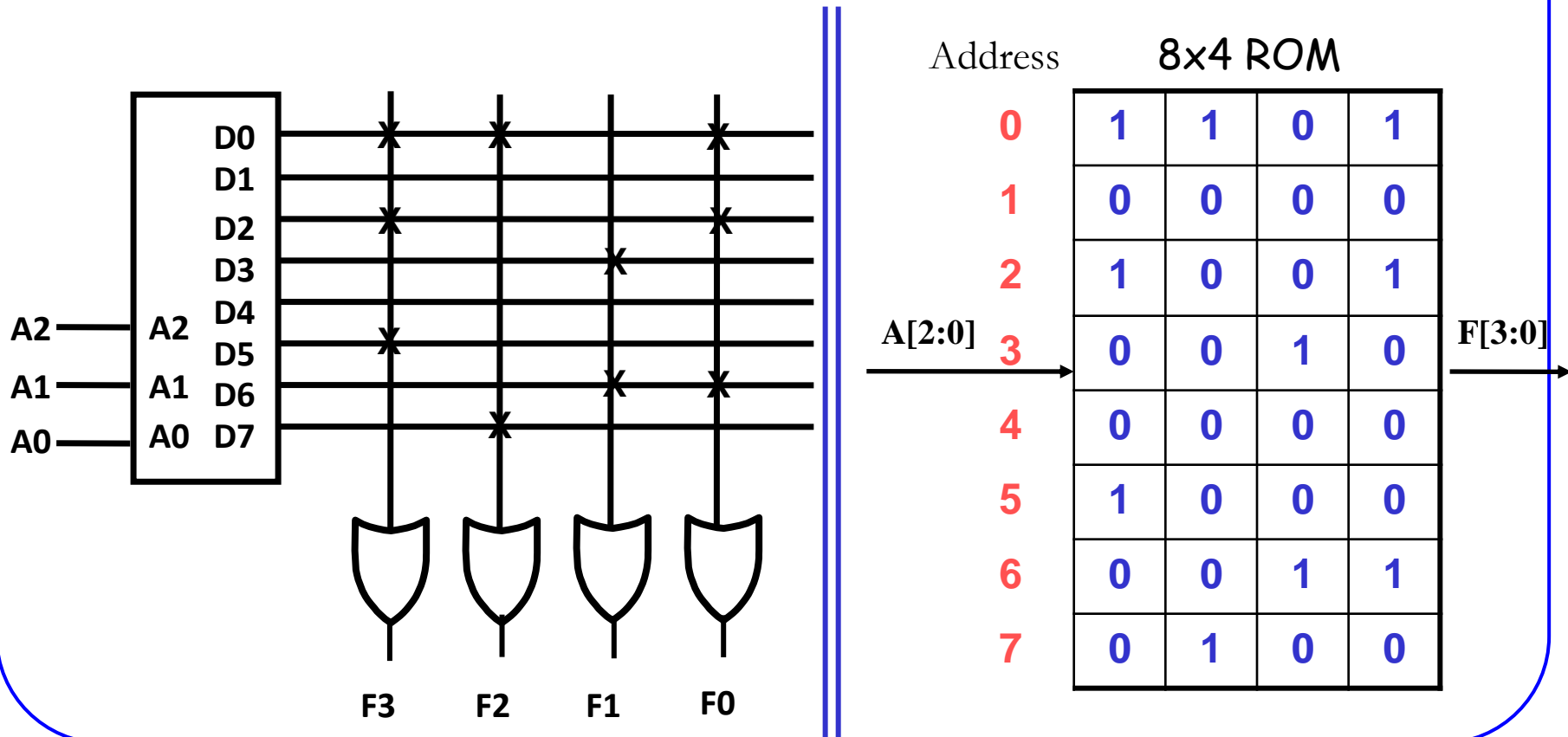
# ROM as Memory (Example)

- **Read Example:** For input  $(A_2, A_1, A_0) = 011$ , output is  $(F_3, F_2, F_1, F_0) = 0010$ .
- What are functions  $F_3, F_2, F_1$  and  $F_0$  in terms of  $(A_2, A_1, A_0)$ ?



# ROM as a Memory

- **History:**

- ROM: the first generation, used as a memory but preprogrammed at the time of manufacturing
- PROM: Programmable ROM, the second generation, able to be programmed at the time of usage
- EPROM: Erasable PROM, able to be erased by UV, and reprogrammed
- EEPROM: Electronically EPROM, able to be erased electronically and reprogrammed

# (Memories)

- **Volatile:**

- Random Access Memory (RAM):
  - SRAM: "static"
  - DRAM: "dynamic"

- **Non-Volatile:**


- ROM
- PROM
- EPROM
- EEPROM
- FLASH memory: similar to EEPROM with programmer integrated on chip

# Design by ROM: Example

- BCD to 7-Segment Display Controller (Decoder)

A B C D	C0	C1	C2	C3	C4	C5	C6
0 0 0 0	1	1	1	1	1	1	0
0 0 0 1	0	1	1	0	0	0	0
0 0 1 0	1	1	0	1	1	0	1
0 0 1 1	1	1	1	1	0	0	1
0 1 0 0	0	1	1	0	0	1	1
0 1 0 1	1	0	1	1	0	1	1
0 1 1 0	1	0	1	1	1	1	1
0 1 1 1	1	1	1	0	0	0	0
1 0 0 0	1	1	1	1	1	1	1
1 0 0 1	1	1	1	0	0	1	1
1 0 1 0	X	X	X	X	X	X	X
1 0 1 1	X	X	X	X	X	X	X
1 1 0 0	X	X	X	X	X	X	X
1 1 0 1	X	X	X	X	X	X	X
1 1 1 0	X	X	X	X	X	X	X
0 1 1 1	X	X	X	X	X	X	X

Reminder:

 


Need a ROM with at least 4 address lines and 7 bits of output

# Design by ROM: Example Continued

- There are some standard devices such as 2764
- Vpp and PGM are used when programming
- Chip Select (CS) and Output Enable (OE) inputs are used to control the chip
- 13 address lines provide  $2^{13}$  (=8192=8K) memory bytes of 8 bits
- Extra address lines grounded
- Extra output line not connected

**2764 EPROM**  
**8K x 8**

 

# ROM vs. PLA/PAL

- **ROM approach advantageous when**
  - (1) design time is short (no need to minimize output functions)
  - (2) little sharing of product terms among output functions
- **ROM problem:**
  - (1) Size doubles for each additional input,
  - (2) Can't use don't cares
- **PLA approach advantageous when**
  - (1) a design tool (like espresso) is available
  - (2) many minterms are shared among the output functions
- **PLA problem:**
  - Too much programmability for ordinary applications => too expensive
- **PAL problem:**
  - Constrained fan-ins on OR planes

# ROM vs. PLA

- **ROM**

- Cheap (high-volume component)
- Medium speed

- **PLA**

- Expensive
  - Complex design; need more sophisticated tools
- Slow
  - Two programmable planes